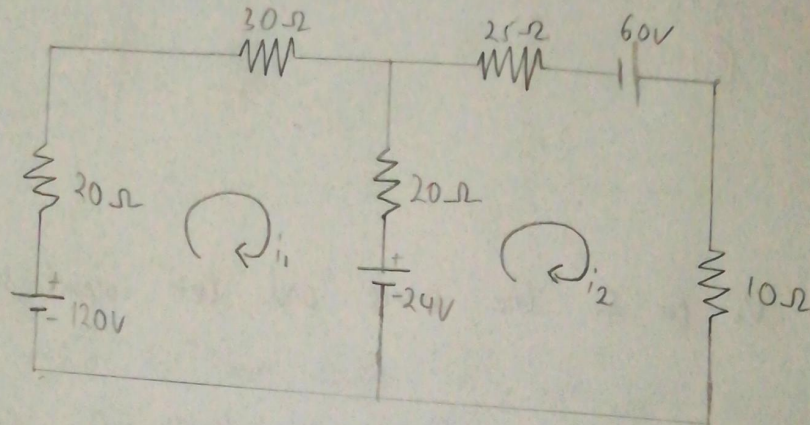


BEEE Digital Assignment -1

Ananta Krishnan B
23BCE1397

1.



Mesh 1:

Let i_1 be the current flowing through mesh 1:

$$120 - 20i_1 - 30i_1 - 20(i_1 - i_2) - 24 = 0 \\ = -70i_1 + 20i_2 = -96 \rightarrow \textcircled{1}$$

Mesh 2:

Let i_2 be the current flowing through mesh 2:

$$24 - 20(i_2 - i_1) - 25i_2 + 60 - 10i_2 = 0 \rightarrow \textcircled{2}$$


Solving equations $\textcircled{1}$ and $\textcircled{2}$, we get:

$$i_1 = 2.017 \text{ A}$$

$$i_2 = 2.260 \text{ A}$$

\therefore Current flowing through the 10Ω resistor $= i_2 = 2.260 \text{ A}$

2.

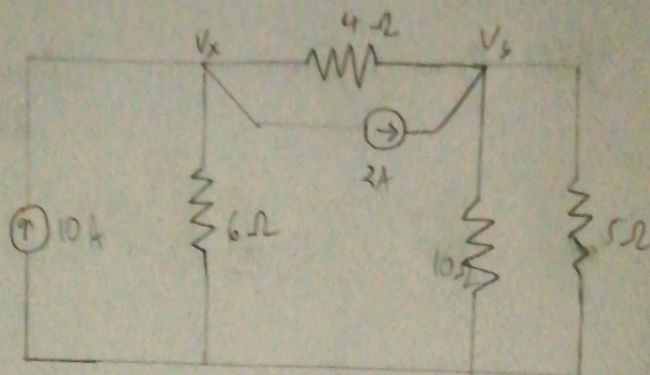

Assume V_x to be the source and let current be flowing out of it

$$\therefore \text{Equation at } x \text{ node} = -10 + \frac{V_x}{6} + 2 + \frac{V_x - V_y}{4} = 0$$

$$= -240 + 4V_x + 48 + 6V_x - 6V_y = 0$$

$$= 10V_x - 6V_y = 192 \rightarrow (1)$$

Next, assume V_y to be the source and let current be flowing out of it.

$$\therefore \text{Equation at } y \text{ node} = \frac{V_y - V_x}{4} - 2 + \frac{V_y}{10} + \frac{V_y}{5} = 0$$

$$= 5V_y - 5V_x - 40 + 2V_y + 4V_y = 0$$

$$= -5V_x + 11V_y = 40 \rightarrow (2)$$

Solving equations (1) and (2), we get:

$$V_x = \underline{29.4V}, V_y = \underline{17V}$$

\therefore Current flowing through resistors:


$$i) 6\Omega = \frac{V_x}{6} = \frac{29.4}{6} = \underline{4.9A}$$

$$ii) 4\Omega = \frac{V_x - V_y}{4} = \frac{12.4}{4} = \underline{3.1A}$$

$$iii) 10\Omega = \frac{V_y}{10} = \frac{17}{10} = \underline{1.7A}$$


$$iv) 5\Omega = \frac{V_y}{5} = \frac{17}{5} = \underline{3.4A}$$

3.

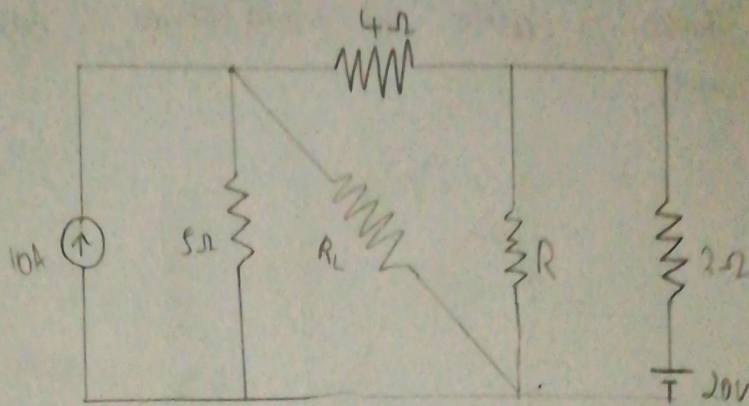

Since the value for the resistor ' R ', we will assume its value to be 2Ω

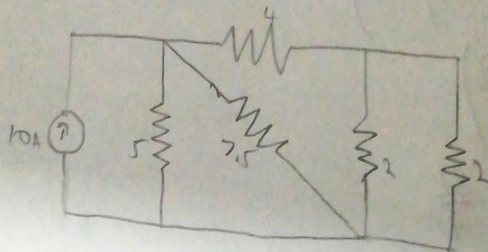i) When current source is active and voltage source is shorted.



$$2\Omega \parallel 2\Omega$$

$$\therefore R_{eq} = \left(\frac{1}{2} + \frac{1}{2} \right)^{-1} = 1\Omega$$

~~1Ω~~ 1Ω in series with 4Ω

$$\therefore R_{eq} = 1 + 4 = 5\Omega$$


$$5\Omega \parallel 5\Omega$$

$$\therefore R_{eq} = \left(\frac{1}{5} + \frac{1}{5} \right)^{-1} = \frac{5}{2} = 2.5\Omega$$

Since $2.5\Omega \parallel 7.5\Omega (R_L)$, we can apply current division rule:

$$I_1 = \frac{I \times 2.5}{2.5 + 7.5} = \frac{10 \times 2.5}{10} = 2.5A \rightarrow \textcircled{1}$$

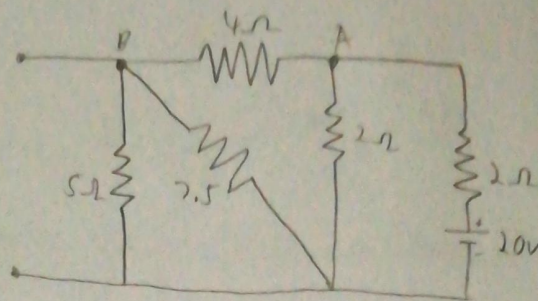i) Voltage source is active and current source is made into an open circuit.



We have to find equivalent resistance - R_{eq}

$$R_{eq} = 2 + \left((4 + 7.5 \parallel 2.5) \parallel 2 \right)$$

$$= 2 + \left((4 + 3) \parallel 2 \right)$$

$$= 2 + \left(7 \parallel 2 \right)$$

$$= 2 + \frac{14}{9} = \frac{32}{9} \Omega$$

$$\therefore \text{Current} = I = \frac{V}{R} = \frac{20}{\left(\frac{32}{9}\right)} = \frac{5 \times 9}{8} = 5.625 \text{ A}$$

At point A, the current going through $4\Omega = I_A$


$$I_A = \frac{I \times 2}{7+2} = \frac{5.625 \times 2}{9} = 1.25 \text{ A}$$

At point B, the current going through $7.5\Omega = I_2$

$$I_2 = \frac{I \times 7.5}{5+7.5} = \frac{1.25 \times 5}{12.5} = 0.5 \text{ A} \quad \text{--- (2)}$$

$$\therefore \text{Total current going through } R_L = I_1 + I_2 = 1.5 + 0.5 = \underline{\underline{3 \text{ A}}}$$


4.

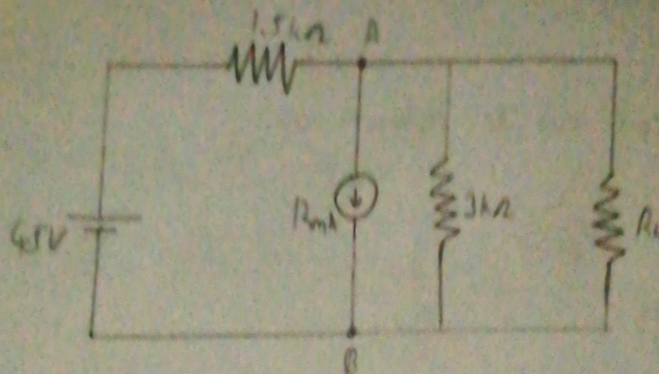

To find thevenin's voltage (V_{TH}), we source transform the current source between A and B.

$$V = IR$$
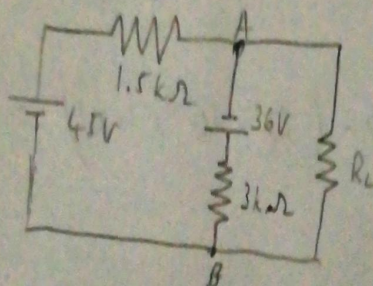
$$= 12 \times 10^{-3} \times 3 \times 10^3 = \underline{\underline{36V}}$$



When we do mesh analysis

$$45 - I \times 1.5 \times 10^3 + 36 - I \times 3 \times 10^3 = 0$$

$$91 = 4.5 \times 10^3 \times I$$

$$I = 18 \times 10^{-3} = \underline{\underline{18mA}}$$

$$\therefore \text{Voltage drop at A} = IR = 18 \times 10^{-3} \times 1.5 \times 10^3 = \underline{\underline{27V}}$$

$$V_A = 45 - 27 = \underline{\underline{18V}}$$


$$V_B = 18 + 36 - (18 \times 10^{-3} \times 3 \times 10^3) = 64 - 54 = \underline{\underline{10V}}$$

$$\therefore \text{Voltage across AB} = V_A - V_B = 27 - 10 = \underline{\underline{17V}}$$

$$\therefore V_{TH} = \underline{\underline{17V}}$$

$$R_{TH} = \left(\frac{1}{3 \times 10^3} + \frac{1}{1.5 \times 10^3} \right)^{-1} = \left(\frac{3}{3 \times 10^3} \right)^{-1} = \underline{\underline{1k\Omega}}$$

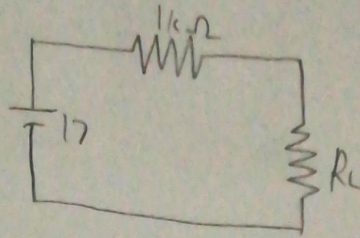Therefore, the circuit can be redrawn as:




When $R_L = 2k\Omega$,

$$R_{eq} = 1k + 2k = 3k\Omega$$

$$\therefore \text{Current } I = \frac{V}{R} = \frac{17}{3} \text{ mA}$$


$$\text{Voltage across } R_L = 17 - \left(\frac{17}{3} \times 10^{-3} \times 1 \times 10^3 \right) = 11.333... \text{ V}$$

5.

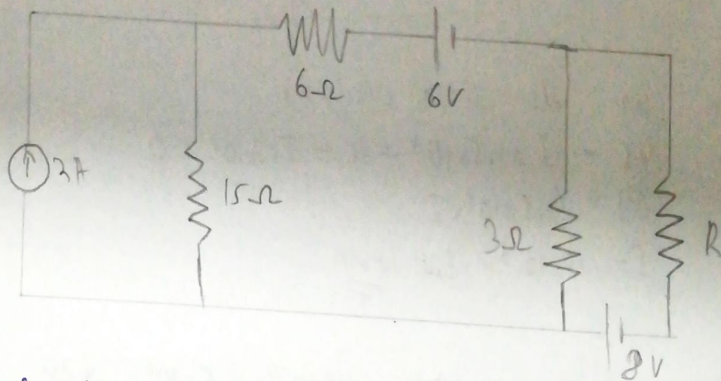

Using source transformation, we can transform the current source to a voltage source.

$$V = IR = 2 \times 15 = 30V$$

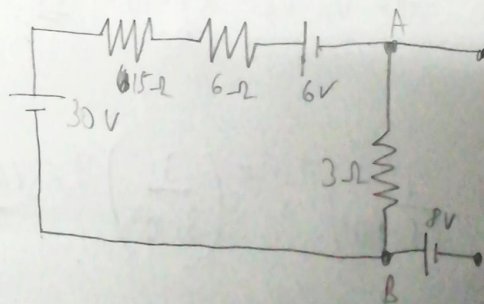

Using mesh analysis:

$$30 - 15i - 6i - 6 - 3i = 0$$

$$24 - 24i = 0$$

$$i = \underline{1A}$$

∴ ~~Voltage~~ Voltage drop at A = $30 - (15 \times 1 + 6 \times 1 + 6) = \underline{3V}$

$$V_A = 3V$$


$V_B = 0 - 8$ (Since an 8V voltage source opposes current)
 $= -8V$

$$\therefore V_{AB} = V_A - V_B = 3 - (-8) = \underline{11V}$$

$$\therefore V_{TH} = 11V$$

$$R_{TH} = \left(\frac{1}{3} + \frac{1}{15+6} \right)^{-1} = \left(\frac{1}{3} + \frac{1}{21} \right)^{-1} = \underline{\underline{\frac{21}{8} \Omega}}$$

∴ The circuit can be redrawn as:

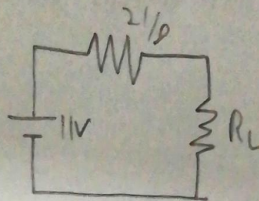

For maximum power, $R_L = R_{TH}$

$$\therefore R_L = \underline{\underline{\frac{21}{8} \Omega}}$$

$$\text{Maximum power} = \frac{V_{TH}^2}{4R_{TH}} = \frac{121}{4 \times \frac{21}{8}} = \frac{121}{\left(\frac{21}{2}\right)} = \frac{121 \times 2}{21} = \underline{\underline{11.523W}}$$

6. We know that for a sinusoidal AC, $V_{rms} = 0.707 V_{max}$
 $\omega = 2\pi f = 2\pi \times 50 = 100\pi \text{ rad/s}$, $V_{max} = 1.414 \times 200 = 282.8 \text{ V}$

\therefore Instantaneous voltage $= v = 282.8 \sin(100\pi t)$

$$V \text{ at } t = 0.0125 \text{ s} = 282.8 \sin(100\pi \times 0.0125)$$

$$= 282.8 \sin\left(\frac{5\pi}{4}\right)$$

$$= 282.8 \times \frac{1}{\sqrt{2}} = \underline{\underline{-200 \text{ V}}}$$

For $V = 141.4 \text{ V}$, $\sin(\omega t) = \frac{1}{2}$ since $282.8 \times \frac{1}{2} = 141.4 \text{ V}$

\therefore ~~at~~ $\omega t = 100\pi t = \frac{\pi}{6}$

$\therefore t = \frac{1}{600} = \underline{\underline{0.001666... \text{ s}}}$

\therefore The maximum positive value of instantaneous voltage will be 141.4 V at $t = \underline{\underline{0.001665 \text{ s}}}$.


7. $R = 5 \Omega$, $L = 31.8 \text{ mH} = \frac{100}{\pi} \text{ mH}$

$X_L = L\omega = \frac{100 \times 10^{-3} \times 2\pi \times 50}{\pi} = 10 \Omega$

$Z = \sqrt{R^2 + X_L^2} = \sqrt{25 + 100} = \sqrt{125} = \underline{\underline{11.180 \Omega}}$

$\therefore \text{Current} = \frac{V}{Z} = \frac{200}{11.180} = \underline{\underline{17.889 \text{ A}}}$

Vector diagram

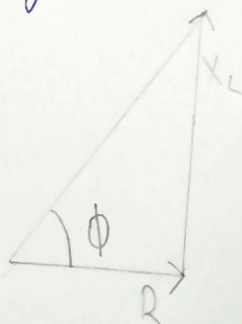

When a non-inductive resistance of $10\ \Omega$ is connected in series with the coil.

$$R = 5 + 10 = 15\ \Omega, \quad X_L = 10\ \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{15^2 + 10^2} = 18.027\ \Omega$$

$$I = \frac{V}{Z} = \frac{200}{18.027} = 11.094\ \text{A}$$

~~Power factor $\phi = \tan^{-1}\left(\frac{X_L}{R}\right)$~~

$$\text{Power factor} = \cos \phi = \frac{R}{Z} = 0.554$$